

PH LAB ASSIGNMENT 4

Name: - Snehal Nalawade

ID: - 202151160

Aim:-

1. Determine the relationship between charge and voltage for a capacitor.
2. Determine the energy stored in a capacitor or a set of capacitors in a circuit.
3. Explore the effect of space and dielectric materials inserted between the conductors of the capacitor in a circuit.
4. Determine the equivalent capacitance of a set of capacitors in series and in parallel in a circuit.

Theory: -

Capacitor: - Ability to store energy in the form of electrical charge.

$$Q = CV,$$

where Q = charge, C = capacitance and V

= Potential difference across the plates

Capacitance: - Ratio of the amount of electric charge stored on a conductor to a difference in electric potential.


$$C = \epsilon_0 A / d$$


where, ϵ_0 = permittivity of free space, A = area of plate, d = distance between plates.

Dielectric inside a capacitor: -

$$C = k \epsilon_0 A / d, \text{ where } k \text{ is Dielectric Constant}$$

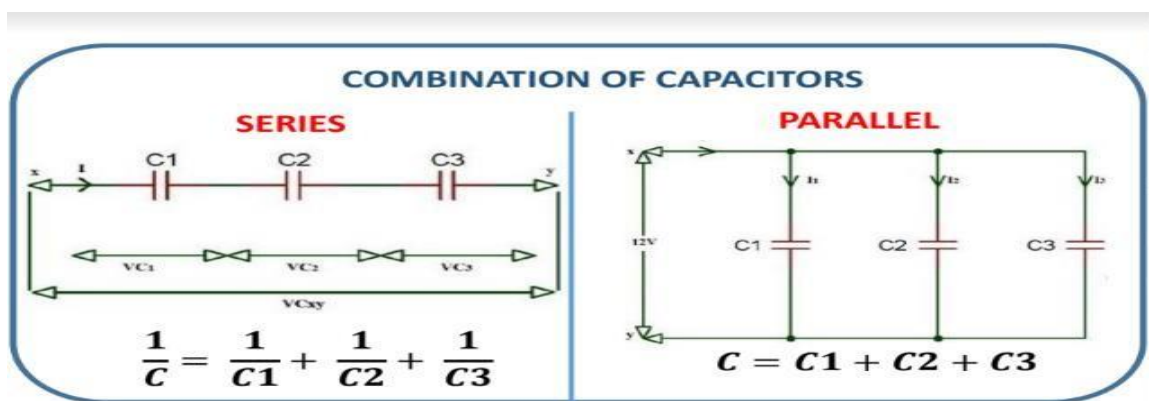Energy stored in a capacitor : - $E = CV^2 / 2$



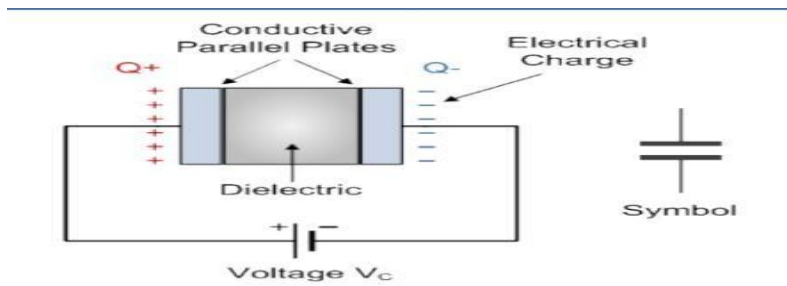

Observation & Tables: -

Table for Aim 1: -

Sr. No.	Voltage	Charge
1	0.172	0.15×10^{-13}
2	0.53	0.47×10^{-13}
3	0.57	0.5×10^{-13}
4	0.65	0.58×10^{-13}
5	0.69	0.61×10^{-13}
6	0.769	0.68×10^{-13}
7	0.849	0.75×10^{-13}
8	0.928	0.82×10^{-13}
9	1.008	0.89×10^{-13}
10	1.088	0.98×10^{-13}

Graph: -

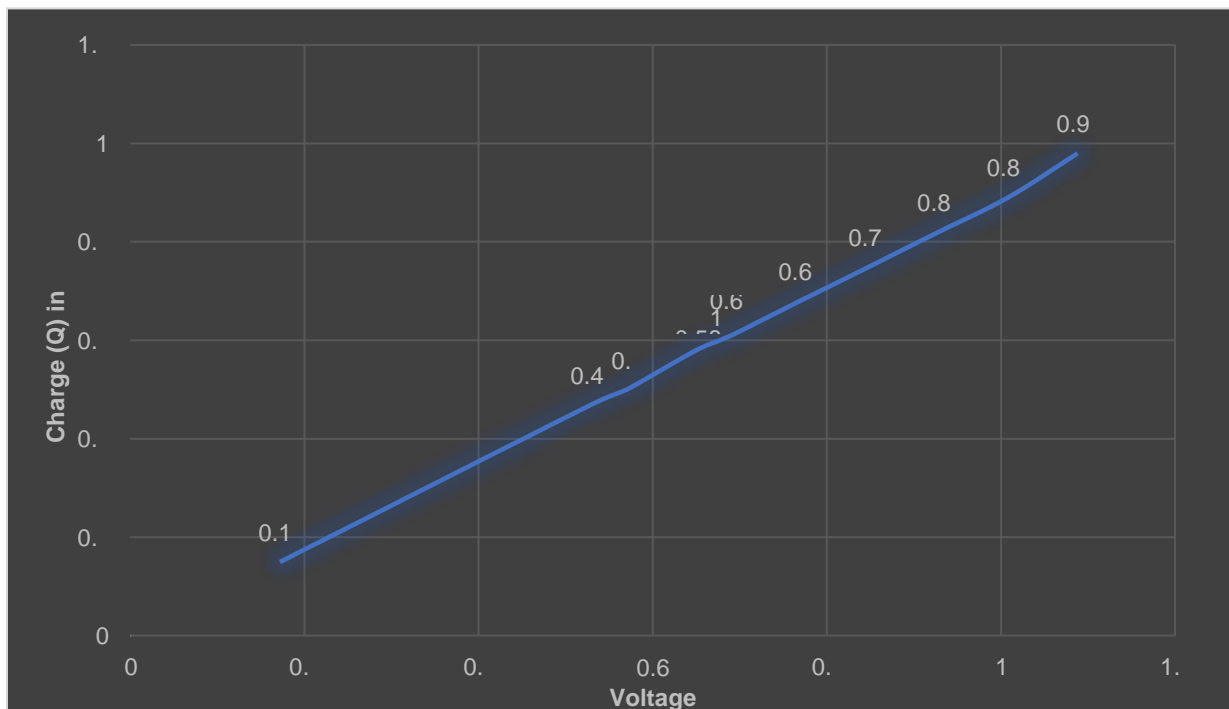


Table for Aim 2: -

Sr. No.	Voltage(V)	Charge (Q)	Stored Energy (J)
1	0.756	0.49×10^{-13}	0.18×10^{-13}
2	1.194	0.77×10^{-13}	0.46×10^{-13}
3	1.5	0.97×10^{-13}	0.73×10^{-13}
4	0.465	0.3×10^{-13}	0.07×10^{-13}
5	0.664	0.49×10^{-13}	0.14×10^{-13}
6	1.102	0.71×10^{-13}	0.39×10^{-13}
7	0.505	0.33×10^{-13}	0.08×10^{-13}
8	0.345	0.22×10^{-13}	0.04×10^{-13}
9	0.903	0.58×10^{-13}	0.26×10^{-13}
10	0.823	0.53×10^{-13}	0.22×10^{-13}

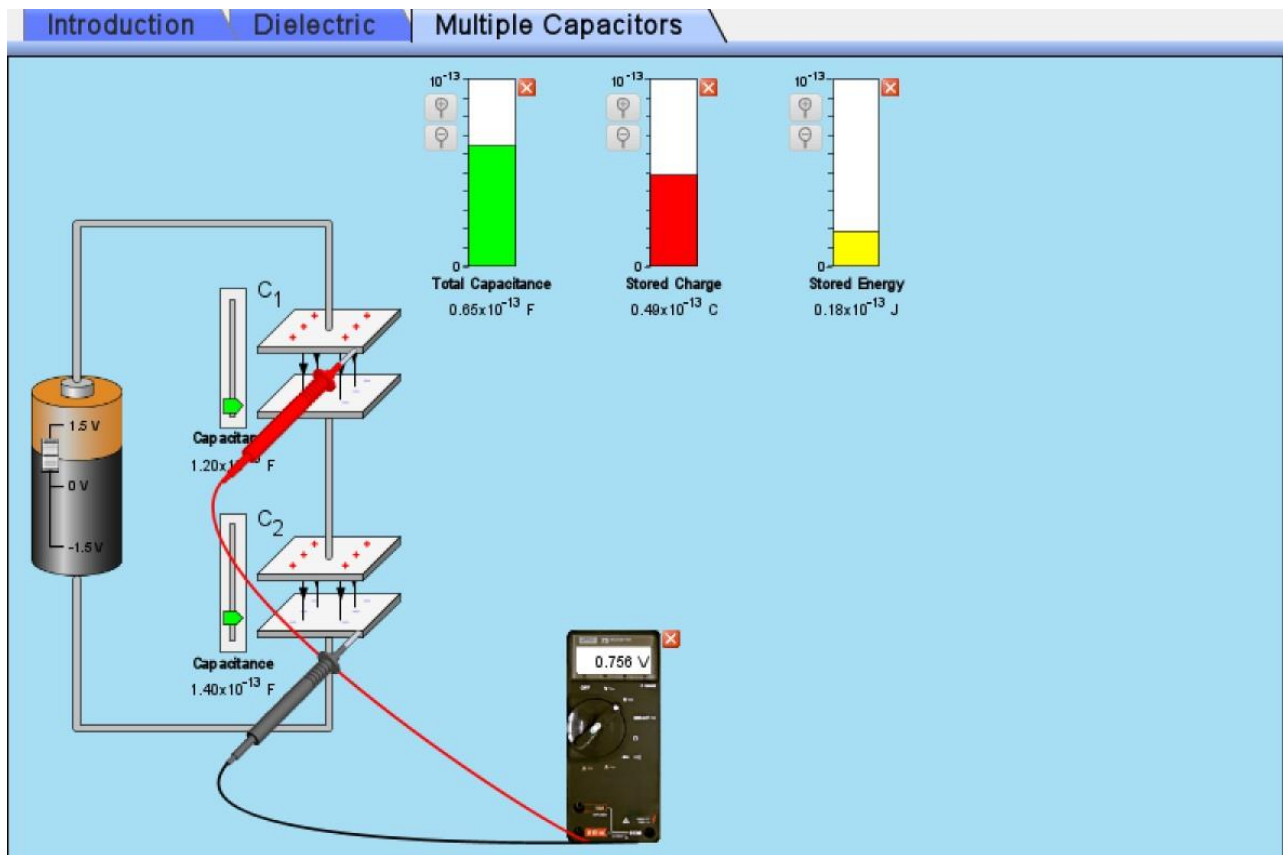


Table for Aim 3: -

Sr. No.	Voltage	Charge	Capacitance	Stored Energy (J)	Dielectric constant
1	0.358	0.67×10^{-13}	0.19×10^{-12}	0.12×10^{-13}	2.1 (Teflon)
2	0.198	0.82×10^{-13}	0.31×10^{-12}	0.06×10^{-13}	3.5 (Paper)
3	0.119	0.5×10^{-13}	0.42×10^{-12}	0.03×10^{-13}	4.7 (Glass)
4	0.279	0.74×10^{-13}	0.27×10^{-12}	0.1×10^{-13}	3 (Custom)
5	0.518	0.91×10^{-13}	0.18×10^{-12}	0.24×10^{-13}	2 (Custom)


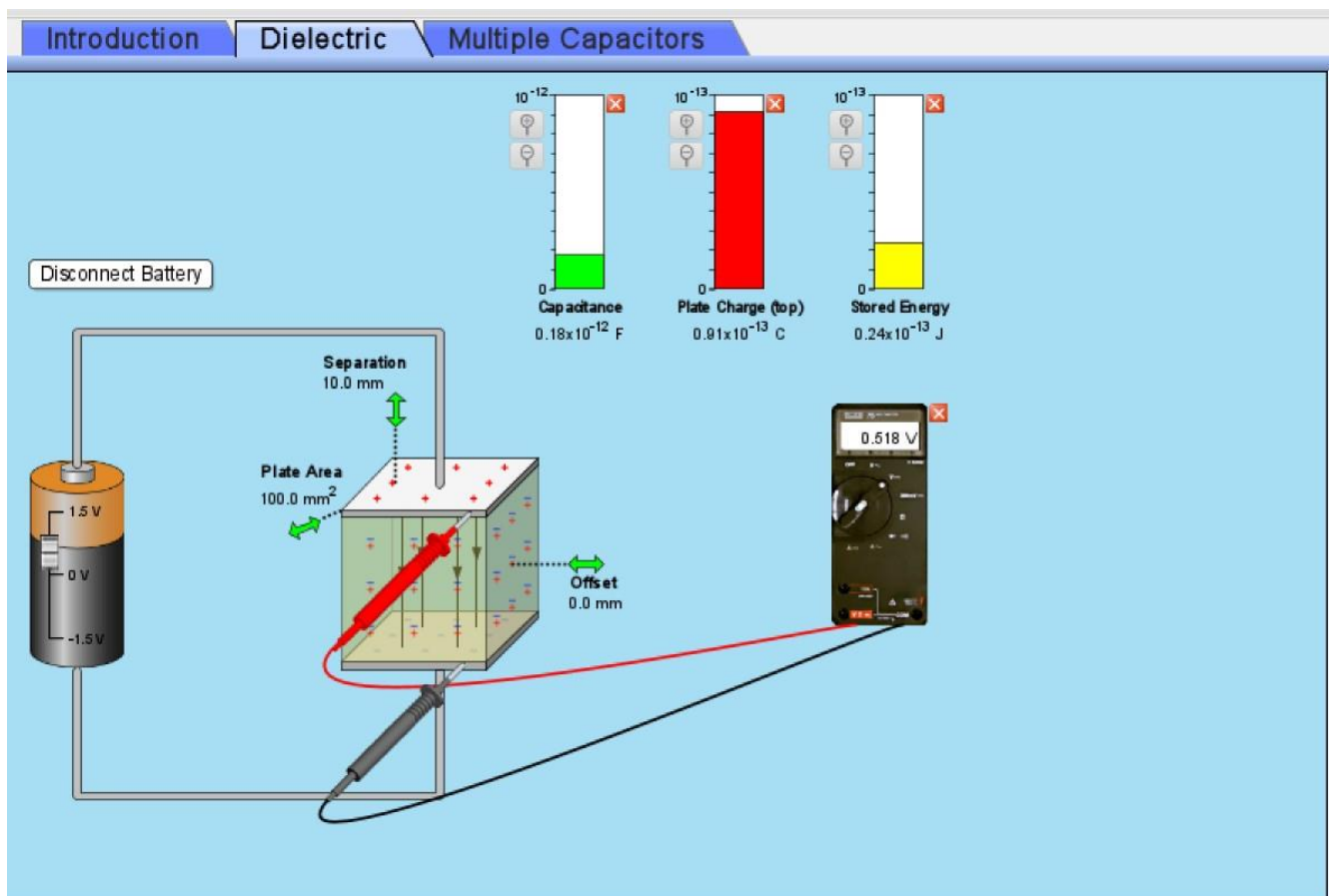


Table for Aim 4: -

Sr. No.	Capacitor 1 (C_1) in F	Capacitor 2 (C_2) in F	Capacitor 3 (C_3) in F	Combination Type	Total Capacitance ($C_{eq.}$)
1	1.5×10^{-13}	1.5×10^{-13}	0	2 In Series	0.07×10^{-12}
2	1.2×10^{-13}	$1.7 \times$	$2.10 \times$	3 In Series	0.05×10^{-12}
3	2×10^{-13}	1.6×10^{-13}	0	2 In Parallel	0.36×10^{-12}
4	2.4×10^{-13}	1.4×10^{-13}	2.2×10^{-13}	3 In Parallel	0.6×10^{-12}
5	2×10^{-13}	1.6×10^{-13}	1.9×10^{-13}	2 In Series + 1 In Parallel	0.28×10^{-12}
6	2×10^{-13}	1.7×10^{-13}	2.5×10^{-13}	2 In Parallel + 1 In Series	0.14×10^{-12}

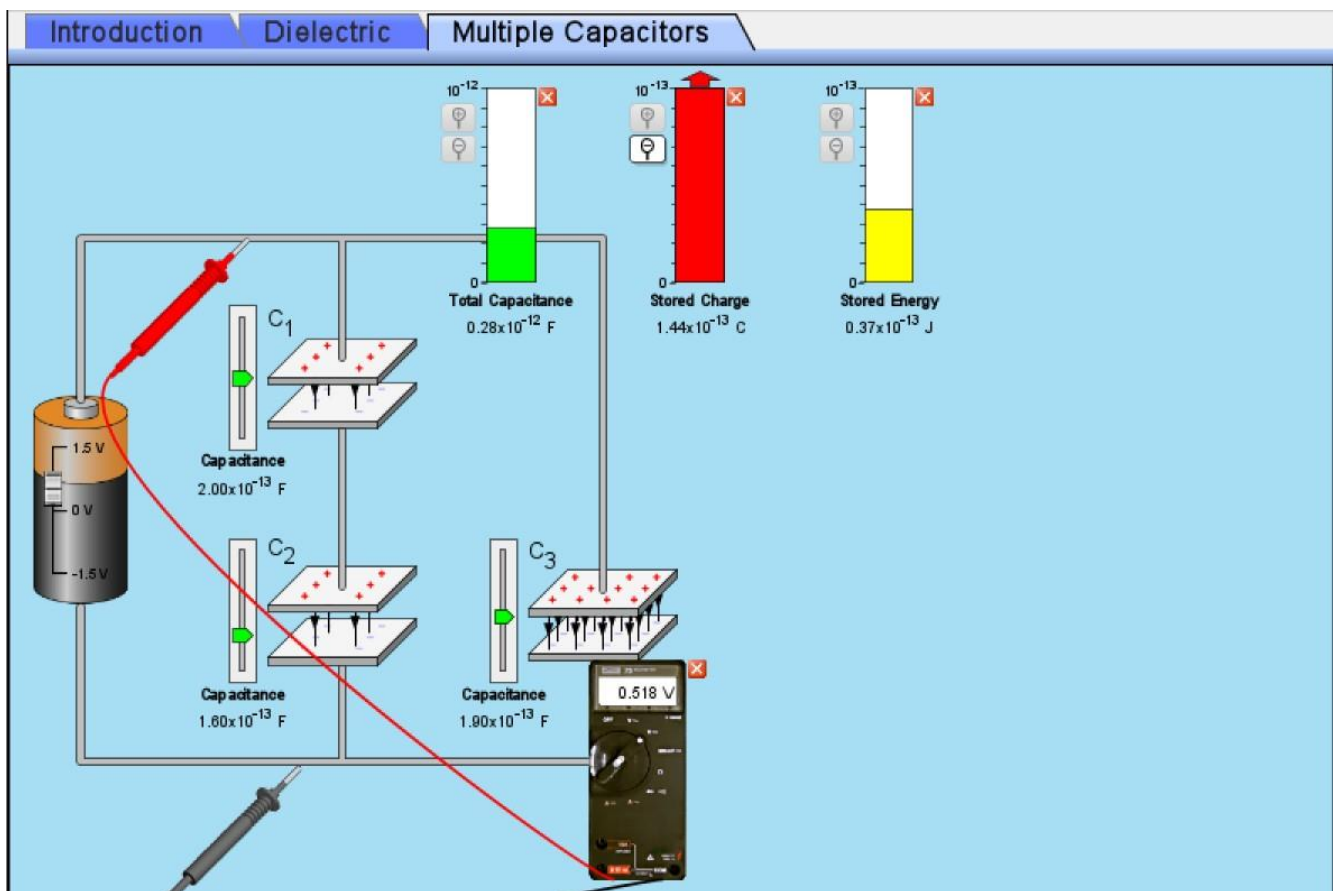

Result: -

In this Experiment we learnt the effect of space and dielectric materials inserted between the conductors of capacitors in a circuit, the relation between charge and voltage for capacitor, the energy stored in a capacitor in a circuit, the equivalent capacitance of a set of capacitors in a series and in parallel in a circuit.

Thank you